

Room: MarleyJF

Name: LastName_FirstName

Please log into Socrative (Either on App or Website) & answer the first question

ECE 211: Electric Circuits

Lesson 5: Circuit Theorems (Part 2)

Text Chapter 4

Prof. Jenny Marley

Lesson Objectives

- Explain the benefits of Thevenin equivalent circuits.
- Apply source transformation to find the equivalent circuit of a circuit between two terminals.
- Find the Thevenin and Norton equivalent circuits between two terminals using only source transformation.
- Find the maximum load power that can be delivered between two terminals.

Review: Branch Current Method

1. Assign currents to each branch using the fewest number of unknowns (in general, you will have n unknowns, where $n = \#$ of meshes - $\#$ current sources)
 - Eg: A circuit with 3 meshes and 1 current source has 2 unknowns (2 unknown branch currents)
2. Assign voltage polarities across resistors
3. Write n KVL equations
4. Solve for unknown branch currents
5. Find any other quantities (depending on the specific problem)

Review: Nodal Analysis


1. Select a reference node
2. Assign node voltages
 - # Unknowns = n = # Nodes – 1 reference – # Voltage sources
3. Apply KCL to write n equations in n unknowns
4. Solve for (unknown) node voltages
5. Answer any questions and/or solve for any other circuit parameters desired

Superposition

What about dependent sources?
They **MUST** remain in the circuit!

- If a circuit has 2 or more **independent** sources, the output is the sum of the partial outputs caused by each source acting along.
- Steps to apply:
 1. Turn off all but 1 **independent** source
 - Current sources look like an open circuit when turned off
 - Voltage sources look like a short circuit when turned off
 2. Analyze the circuit to find the output for only that 1 independent source; this is one partial output
 3. Repeat for each source
 4. Total output = \sum partial outputs (eg $V_0 = V_{01} + V_{02} + \dots + V_{0n}$)

Thevenin's Theorem

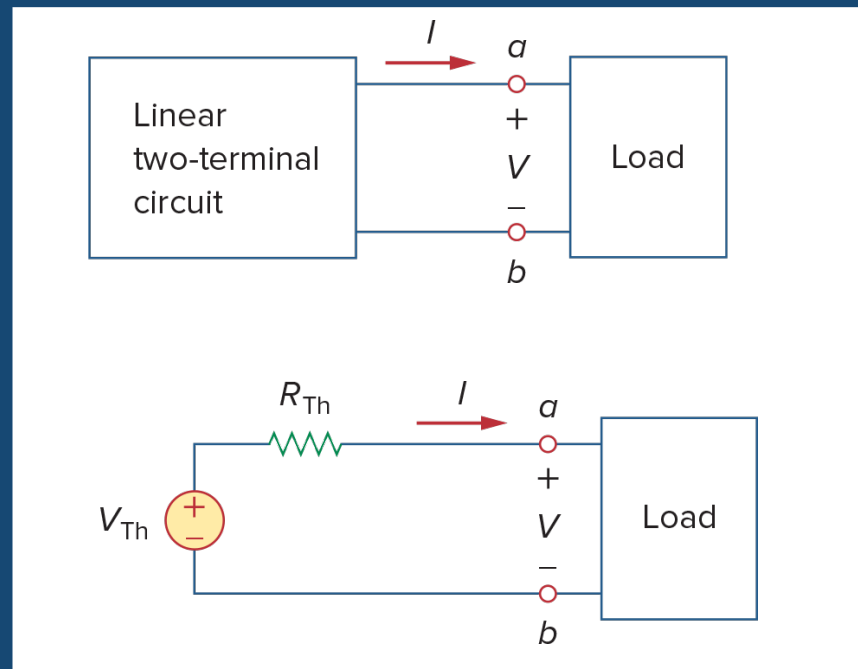


- Any linear, 2-terminal device (i.e. circuit) can be replaced with a voltage source equal to the **open circuit voltage** in series with a resistor equal to the resistance 'looking in' with all independent sources OFF.

Steps to find Thevenin equivalent circuit

1. Find the Thevenin voltage, V_T , by analyzing your circuit to find the voltage across the terminals of your device.
2. Find the Thevenin resistance, R_T , by turning OFF all **independent** sources and finding the equivalent resistance 'seen' between the terminals of your device.
 - If you only have independent sources, you are left with a resistor network.
 - If you have dependent sources, you must use a test source across the terminals of your device and then use Ohm's Law to find the resistance. NEVER take out dependent sources when finding R_T .
3. Draw your equivalent circuit between the terminals of your device. This is a voltage source in series with a resistor.

Norton's Theorem

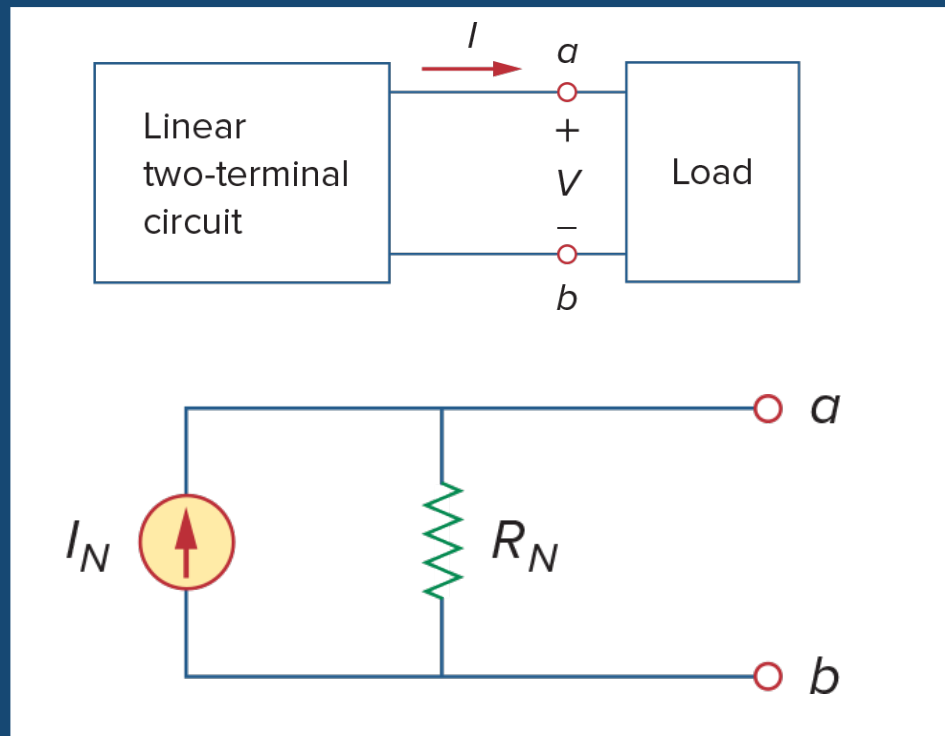

Notice:


$$R_T = R_N = R_{eq}$$

- Any linear 2-terminal circuit can be replaced with a current source equal to the **short circuit current** in parallel with a resistor equal to the resistance looking in with all **independent** sources OFF.

Steps to find Norton equivalent circuit

1. Find the Norton current, I_N , by analyzing your circuit to find the short-circuit current between the terminals of your device.
2. Find the Norton resistance, R_N , by turning OFF all **independent** sources and finding the equivalent resistance 'seen' between the terminals of your device.
 - If you only have independent sources, you are left with a resistor network.
 - If you have dependent sources, you must use a test source across the terminals of your device and then use Ohm's Law to find the resistance. NEVER take out dependent sources when finding R_N .
3. Draw your equivalent circuit between the terminals of your device. This is a current source in parallel with a resistor.


Source Transformation

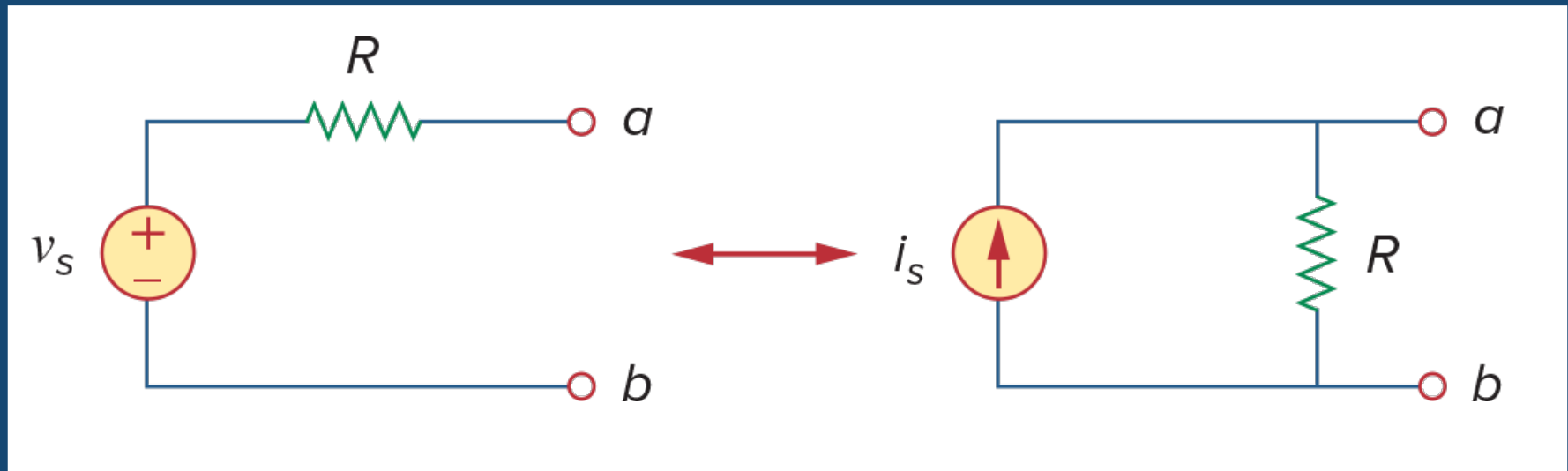

- $V_S = I_S R$

Recap: Find the Thevenin resistance

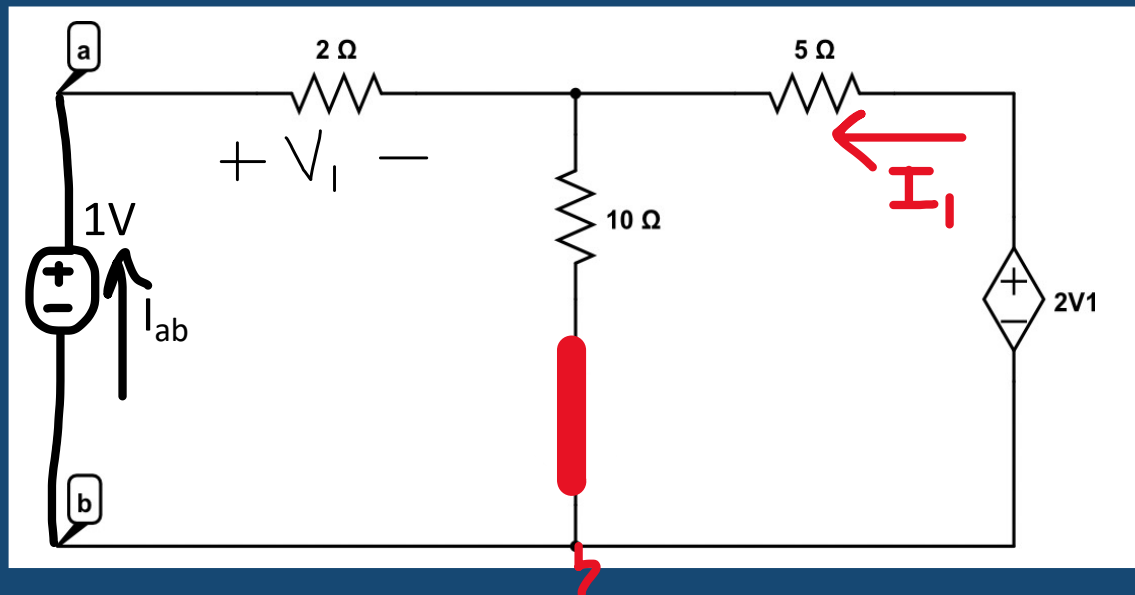- Did I have to use a current source? No! Try a voltage source:



- KVL Left: $-1 + 2I_{ab} + 10(I_1 + I_{ab}) = 0$
 - KVL Right: $-10(I_1 + I_{ab}) - 5I_1 + 4I_{ab} = 0$
- $\rightarrow I_1 = -1/20 \text{ A}, I_{ab} = 1/8 \text{ A} \rightarrow 1 \text{ A} = I_{ab} R_T \rightarrow R_T = 8 \Omega \checkmark$


Why Thevenin?

Why Thevenin?

- If we are only interested in what's happening (i.e. things like voltage, current, power, etc) between terminals a and b , then we can **greatly** simplify our analysis by replacing the rest of the circuit with its Thevenin (or Norton!) equivalent.
- We also might only be interested in a single subsystem within our circuit.
- It turns out that it also tells us something about how to transmit the **maximum** power to a load between terminals a and b .


Load Power

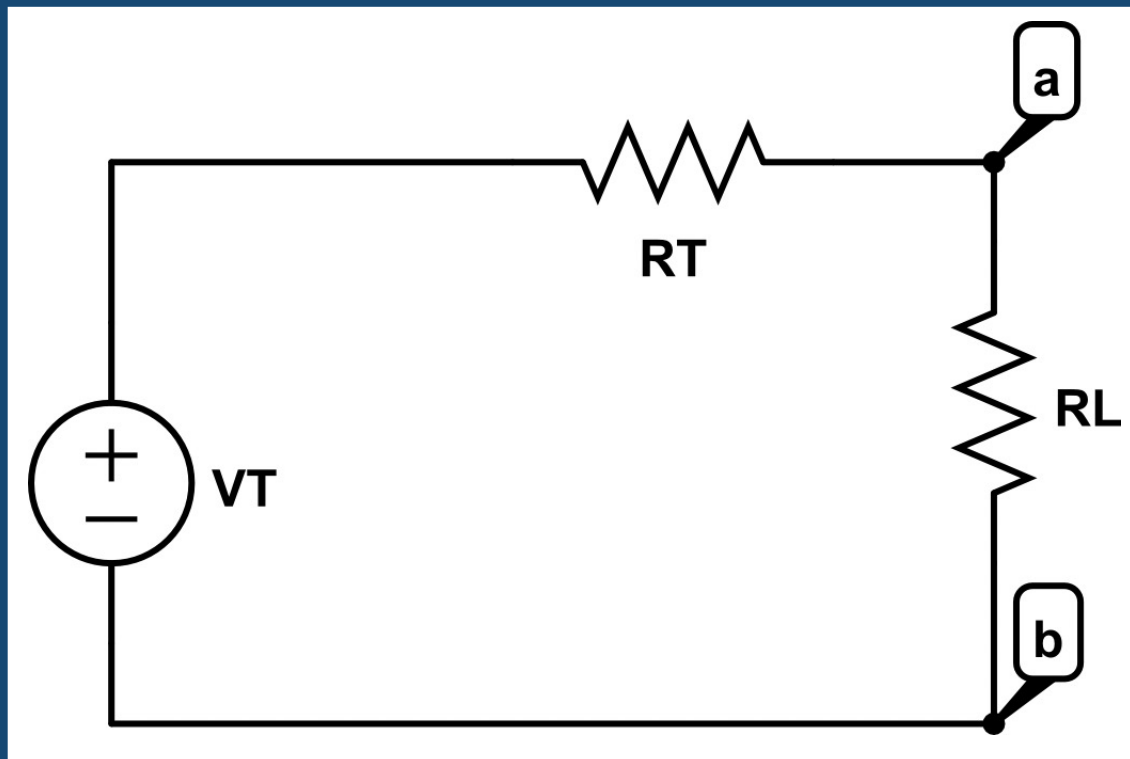- Consider a Thevenin equivalent circuit with an unknown resistive load R_L connected to it.



Load Power

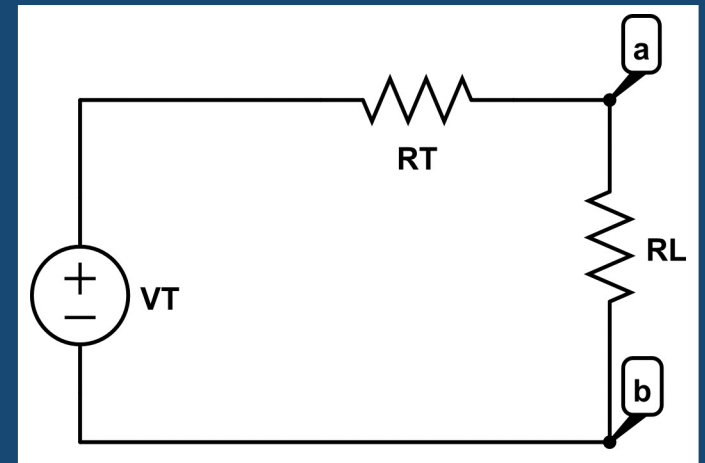
- Consider a Thevenin equivalent circuit with an unknown resistive load R_L connected to it.
- Find an expression for R_L 's power in terms of V_T , R_T , and R_L :



Load Power

- Consider a Thevenin equivalent circuit with an unknown resistive load R_L connected to it.
- Find an expression for R_L 's power in terms of V_T , R_T , and R_L :
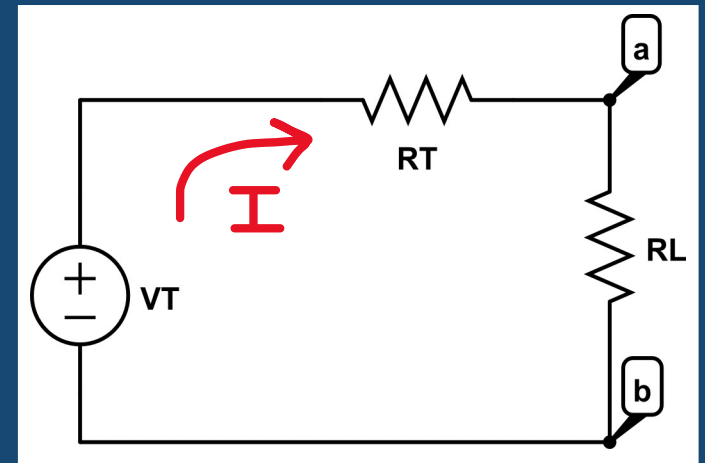
$$P_L = I^2 R_L = \left(\frac{V_T}{R_T + R_L} \right)^2 R_L = \frac{R_L}{(R_T + R_L)^2} V_T^2$$




Load Power

- Consider a Thevenin equivalent circuit with an unknown resistive load R_L connected to it.
- Find an expression for R_L 's power in terms of V_T , R_T , and R_L :

$$P_L = I^2 R_L = \left(\frac{V_T}{R_T + R_L} \right)^2 R_L = \frac{R_L}{(R_T + R_L)^2} V_T^2$$

- What if $R_L = 0 \Omega$?

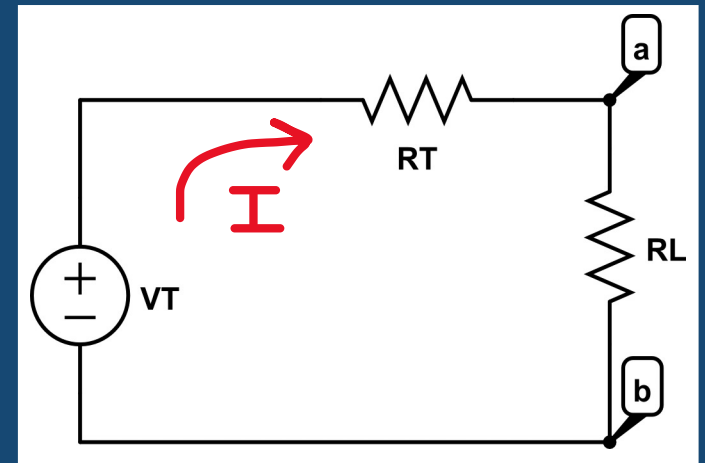


Load Power

- Consider a Thevenin equivalent circuit with an unknown resistive load R_L connected to it.
- Find an expression for R_L 's power in terms of V_T , R_T , and R_L :

$$P_L = I^2 R_L = \left(\frac{V_T}{R_T + R_L} \right)^2 R_L = \frac{R_L}{(R_T + R_L)^2} V_T^2$$

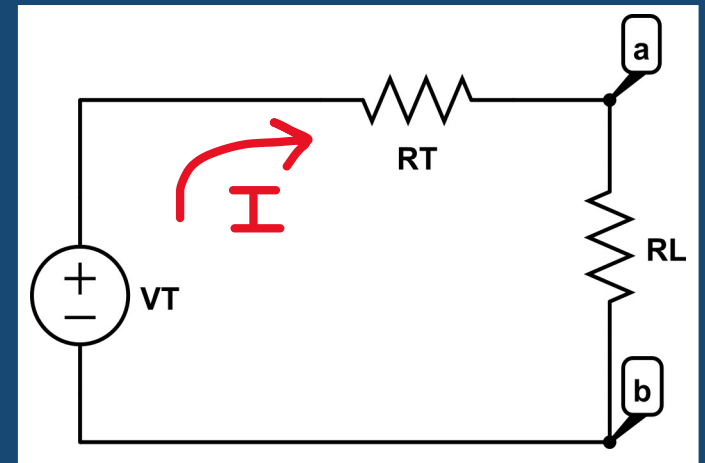- What if $R_L = 0 \Omega$? $P_L = 0 \text{ W}$
- What if $R_L \rightarrow \infty \Omega$?




Load Power

- Consider a Thevenin equivalent circuit with an unknown resistive load R_L connected to it.
- Find an expression for R_L 's power in terms of V_T , R_T , and R_L :

$$P_L = I^2 R_L = \left(\frac{V_T}{R_T + R_L} \right)^2 R_L = \frac{R_L}{(R_T + R_L)^2} V_T^2$$

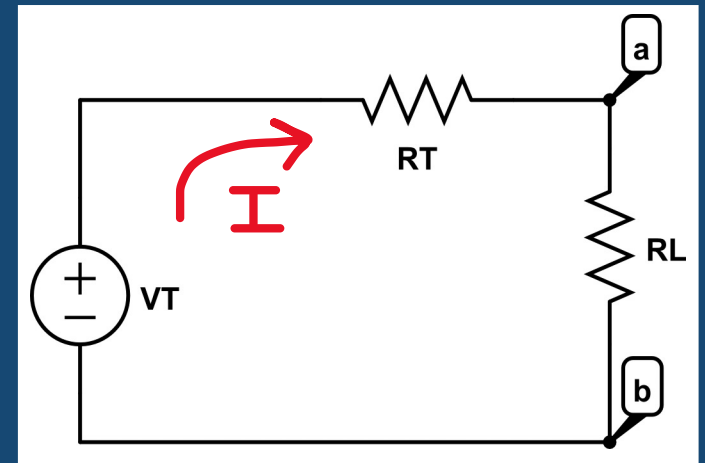- What if $R_L = 0 \Omega$? $P_L = 0 \text{ W}$
- What if $R_L \rightarrow \infty \Omega$? $P_L = 0 \text{ W}$
- What about in between?




Maximum Power Graphically: Zoomed In

- Let $V_T = 2\text{ V}$, $R_T = 5\ \Omega$ and graph P_{RL} vs R_L :

At what load resistance does the maximum power occur?

$$R_L = 5\ \Omega = R_T !$$

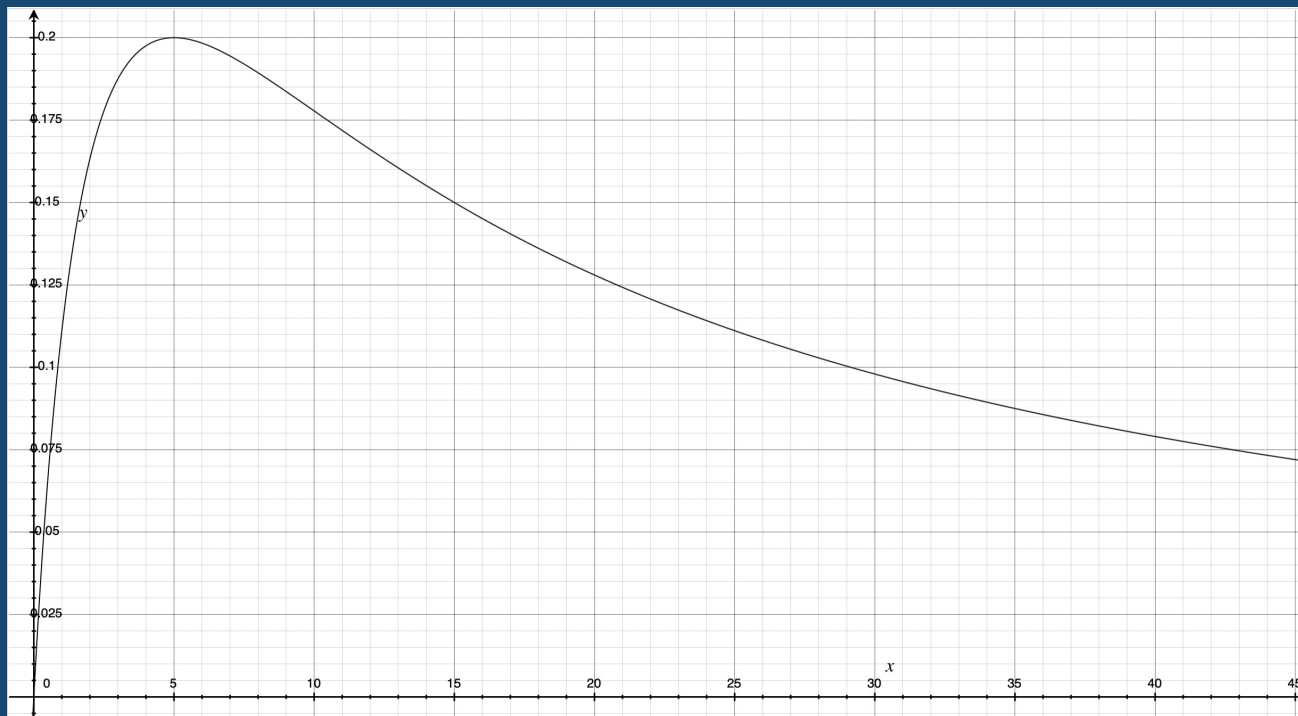

R_L (Ω)

But Why?

- Recall that we found the relationship $P_L = \frac{R_L}{(R_T + R_L)^2} V_T^2$, which is a function of R_L with known parameters R_T and V_T .
- How do we find the maximum of a function?

But Why?

- Recall that we found the relationship $P_L = \frac{R_L}{(R_T + R_L)^2} V_T^2$, which is a function of R_L with known parameters R_T and V_T .
- How do we find the maximum of a function?

$$\frac{dP_L}{dR_L} = V_T^2 \left[\frac{(R_T + R_L)^2 - R_L(2(R_T + R_L))}{(R_T + R_L)^4} \right] = 0$$

$$\frac{dP_L}{dR_L} = V_T^2 \left[\frac{(R_T + R_L) - R_L(2)}{(R_T + R_L)^3} \right] = 0 \rightarrow \frac{(R_T + R_L) - R_L(2)}{(R_T + R_L)^3} = 0 \rightarrow \frac{(R_T - R_L)}{(R_T + R_L)^3} = 0$$

$$\rightarrow \mathbf{R_T = R_L}$$

Summary

- Thevenin equivalent circuits allow us to simplify circuit analysis and/or easily calculate the maximum load power that can be delivered between two terminals.
- The maximum transferred power to a load occurs when $R_L = R_T$.
- Source transformation allows us to convert a current source in parallel with a resistor to an equivalent voltage source in series with the same resistance.